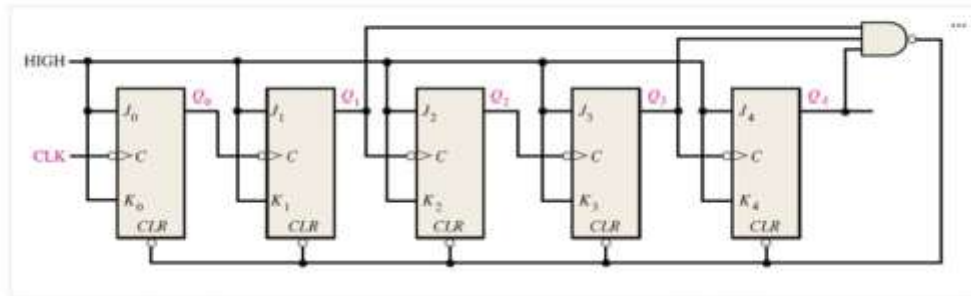


JK FLIPFOP FREQUENCY ANSWR

The frequency of the clock waveform input to the circuit shown below is 10 MHz. determine the frequency, in kHz, of the output waveform at Q_4 . Round your answer to the nearest whole number.



Round your answer to 0 decimal places.

Your answer: 4

Incorrect

The answer is 385

Theory


- In **Synchronous operation**: All flip-flops receive the **same clock**, eliminating ripple-delay (all outputs change together) therefore the flip flops are synchronised
- **Truncated sequence**

Asynchronous Decade Counters

The **modulus** of a counter is the number of unique states through which the counter will sequence. The maximum possible number of states (maximum modulus) of a counter is 2^n , where n is the number of flip-flops in the counter. Counters can be designed to have a number of states in their sequence that is less than the maximum of 2^n . This type of sequence is called a *truncated sequence*.

- They also know as Modulo counters (MOD-N): These counters out up to a predefined number N and then reset to Zero
- They do not run the full 2^n states
- So they can run the full states but sometimes we change that as in make the restart earlier
- As we observe the J-K flipflop we can see a few things which is the
 - All JKs are tied $J=K=1 \rightarrow$ they toggle on every clock edge.

Truth Table			
J	K	CLK	Q
0	0	↑	Q_0 (no change)
1	0	↑	1
0	1	↑	0
1	1	↑	$\overline{Q_0}$ (toggles)

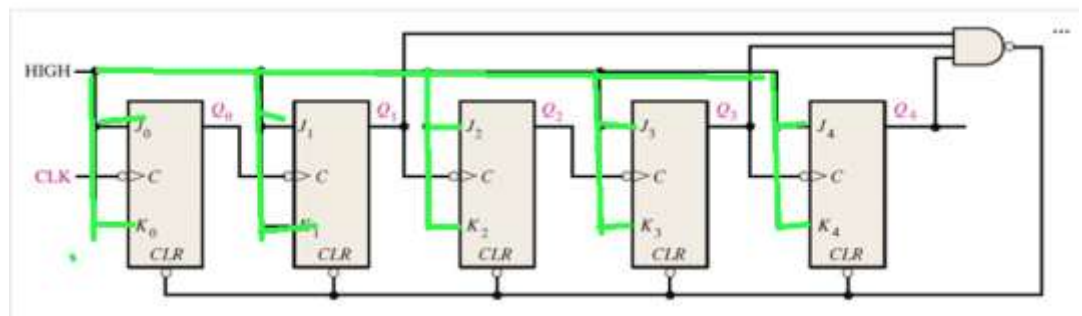

- The **CLR** pin has a little **bubble (small circle)** at its input.
 - That bubble means the input is **active-LOW**.



- In simple terms to activate the clear we have to input a low which is a zero
- This will clear the flipflops (Restart them)
- Now look at the and gate

3-Input NAND Gate



Truth Table			
Input A	Input B	Input C	$X = (A.B.C)'$
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

- It only gives us a 0 when all inputs are high
- The output of the NAND gate is connected to clear of all the flipflops
- So at the point where the NAND gate receives all 1s then it will restart the count

- The inputs to the gate are Q1, Q3, Q4 when all of them are one that's when the count will restart
 - To get the limit in decimal we set the all Q pins to 0 except the one connected to the NAND gate do from Q4-Q0 (MSB-LSB)
 - 11010 which is 26 in decimal that is the limit
- The counter counts from 00000 (0) up to 11001 (25)
- At 11010 (26), the AND gate activates → drives CLR LOW → all FFs reset to 0.
- This makes the counter repeat every 26 cycles.

Frequency division

Further division of a clock frequency can be achieved by using the output of one flip-flop as the clock input to a second flip-flop, as shown in Figure 7-37. The frequency of the Q_A output is divided by 2 by flip-flop B. The Q_B output is, therefore, one-fourth the frequency of the original clock input. Propagation delay times are not shown on the timing diagrams.

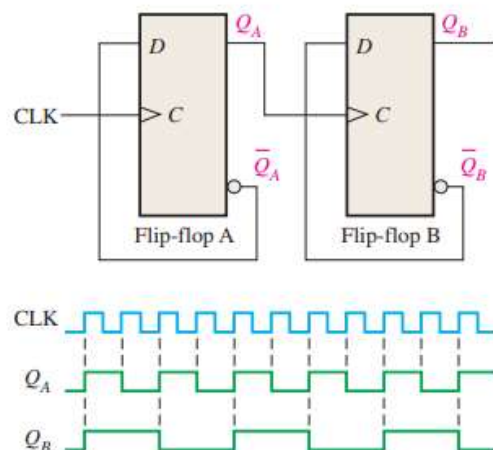



FIGURE 7-37 Example of two D flip-flops used to divide the clock frequency by 4. Q_A is one-half and Q_B is one-fourth the frequency of CLK. Open file F07-37 and verify the operation.




By connecting flip-flops in this way, a frequency division of 2^n is achieved, where n is the number of flip-flops. For example, three flip-flops divide the clock frequency by $2^3 = 8$; four flip-flops divide the clock frequency by $2^4 = 16$; and so on.

EXAMPLE 7-9

Develop the f_{out} waveform for the circuit in Figure 7-38 when an 8 kHz square wave input is applied to the clock input of flip-flop A.

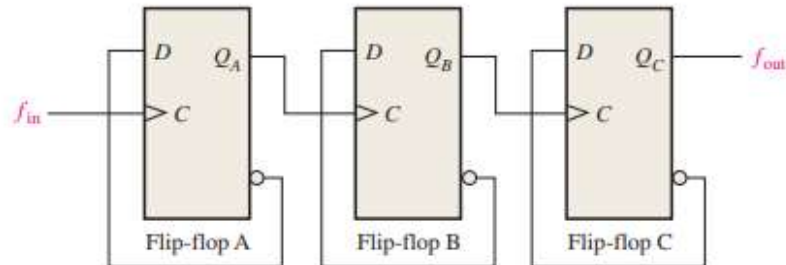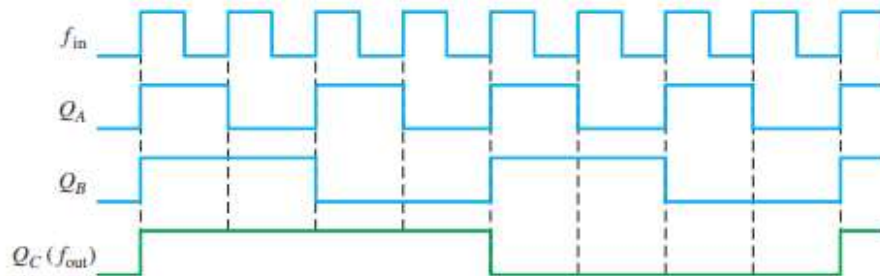**FIGURE 7-38****Solution**

The three flip-flops are connected to divide the input frequency by eight ($2^3 = 8$) and the Q_C (f_{out}) waveform is shown in Figure 7-39. Since these are positive edge-triggered flip-flops, the outputs change on the positive-going clock edge. There is one output pulse for every eight input pulses, so the output frequency is 1 kHz. Waveforms of Q_A and Q_B are also shown.


**FIGURE 7-39****Related Problem**

How many flip-flops are required to divide a frequency by thirty-two?

Therefore

$$\text{output frequency} = \frac{\text{input clock}}{\text{modulus}}$$

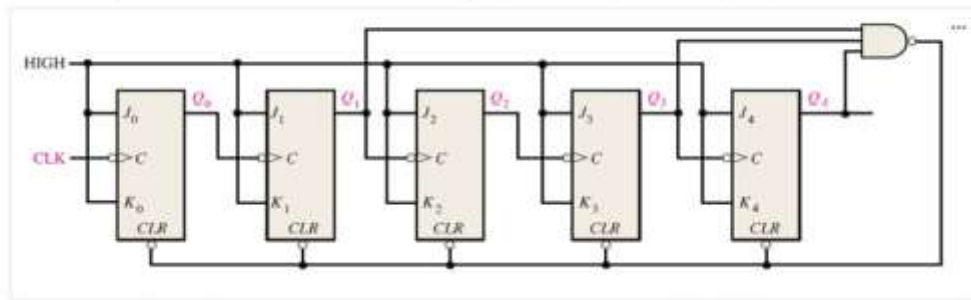The frequency of the clock waveform input to the circuit shown below is 10 MHz. determine the frequency, in kHz, of the output waveform at Q_4 . Round your answer to the nearest whole number.



Round your answer to 0 decimal places.

Your answer: 4

Incorrect

The answer is 385

ANSWER

$$\text{output frequency} = \frac{\text{input clock}}{\text{modulus}} = \frac{10\text{Mhz}}{26} = 384615.3846 = 384.615 \times 10^3 = 385\text{Khz}$$

19:14



Test

Correct

The answer is 3

8


CALCULATED FORMULA

0 / 7



INCORRECT

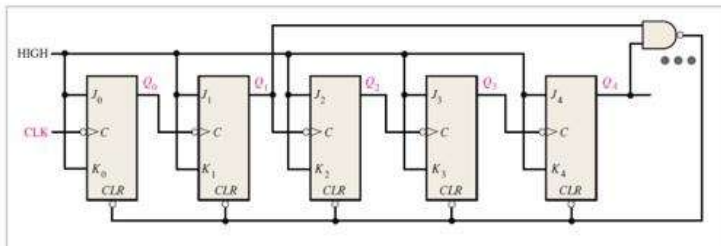The frequency of the clock waveform input to the circuit shown below is 11 MHz. determine the frequency, in kHz, of the output waveform at Q_4 . Round your answer to the nearest whole number.



Round your answer to 0 decimal places.

Your answer: 344

Incorrect

The answer is **611**

9


CALCULATED NUMERIC

0 / 10



INCORRECT

- Two input nand gate

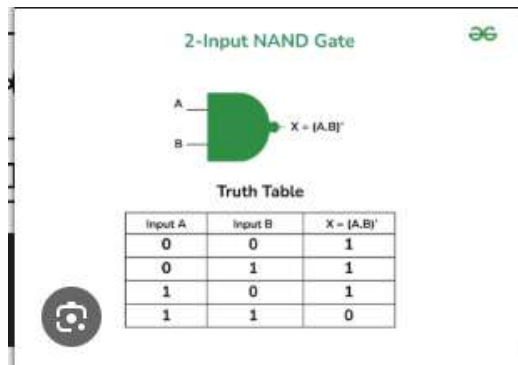

- Q1& Q4 must be 1 to clear
- MSB-LSB 10010
- DEC = 18

ANSWER

$$output frequency = \frac{input\ clock}{modulus} = \frac{11Mhz}{18} = 611111.111 = 611.11110^3 = 611Khz$$